

# Day 6 (Feb 3rd)

Monday, February 3, 2020 1:37 PM

## Division

Step	A (8 bit)	Q (9 bit)	Divisor (And Calculation)
0	0000 0000	1 0001 0010	0000 1101
1	0000 0001	0 0010 0100	A < D
2	0000 0010	0 0100 1000	A < D
3	0000 0100	0 1001 0000	A < D
4	0000 1000	1 0010 0000	A < D
5	0001 0001	0 0100 0000	A > D (A-D = 100)
5.5	0000 0100	0 0100 0001	Move A-D to A and put a 1 as next bit
6	0000 1000	0 1000 0010	A < D
7	0001 0000	1 0000 0100	A > D (A-D = 11)
7.5	0000 0011	1 0000 0101	Move A-D to A and put a 1 as next bit
8	0000 0111	0 0000 1010	A < D
9	0000 1110	0 0001 0100	A > D (A-D = 1)
9.5	0000 0001	0 0001 0101	Move A-D to A and put a 1 as next bit Lastly. 273 with a Remainder of 1

Demultiplexer is in photos

S	I	A	B
0	0	0	0
0	1	1	0
1	0	0	0
1	1	0	1

$$A = S' * I$$

$$B = S * I$$

Comparator

Returns is  $A < B$ ,  $A > B$ ,  $A == B$

All Four Nor Gates are 1 then  $A == B$

Most Significant  $A > MS$  of  $B$  then  $A > B = \text{true}$

More Significant Overrides bits down the line

A	B	$A'$	$B'$	$A'B$	$AB'$	+ (Equality)	$+'$
0	0	1	1	0	0	0	1
0	1	1	0	1	0	1	0
1	0	0	1	0	1	1	0
1	1	0	0	0	0	0	1

$$F = \sum(2, 7, 8, 12, 13)$$

d (don't cares) =  $\sum(1, 4, 5, 10)$

			C	C	
	0	x	0	1	
	x	x	1	0	B
A	1	1	0	0	B
A	0	1	0	x	
		D	D		

$$F = B' * C * D' \text{ (2 and 10)} + D * C' \text{ (1,5,9,13)} + B * C' \text{ (4,5,12, and 13)} + BDA' \text{ (5 and 7)}$$

Fastest Choices NAND - NAND or NOR - NOR

NAND - NAND

Step	Equation	Law
0	$[(B'C'D)' * (DC')' * (BC')' * (BDA')']'$	Demorgans

NOR-NOR

$$F' = AC + A'C' + \{ D'C'B', AB'D' \} + \{ BA'D', CBD' \} + \{ B'CD, A'B'D \}$$

$$F = (F')' = ( AC + A'C' + \{ D'C'B', AB'D' \} + \{ BA'D', CBD' \} + \{ B'CD, A'B'D \} )'$$

$$A*C = (A'+C')' \text{ To turn the And into a NOR}$$

$$F = [(A'+C')' + (A+C)' + (\dots)']'$$

Make Sure To List Choices

Side Note: Layout for 3 variables

			B	B
A				
		C	C	